

## 8. RLC CIRCUITS

**8.1. Series RLC Circuits.** Electric circuits provide an important example of linear, time-invariant differential equations, alongside mechanical systems. We will consider only the simple series circuit pictured below.

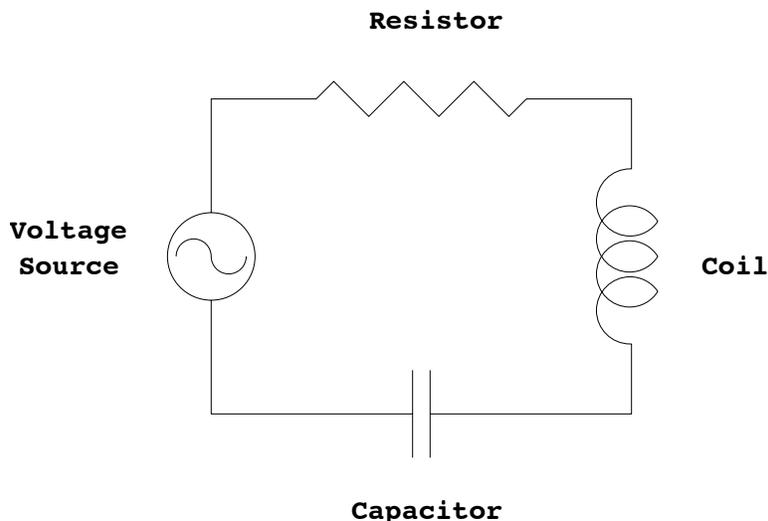


FIGURE 5. Series RLC Circuit

The Mathlet **Series RLC Circuit** exhibits the behavior of this system, when the voltage source provides a sinusoidal signal.

Current flows through the circuit; in this simple loop circuit the current through any two points is the same at any given moment. Current is denoted by the letter  $I$ , or  $I(t)$  since it is generally a function of time.

The current is created by a force, the “electromotive force,” which is determined by voltage *differences*. The voltage *drop* across a component of the system *except for the power source* will be denoted by  $V$  with a subscript. Each is a function of time. If we orient the circuit consistently, say clockwise, then we let

$V_L(t)$  denote the voltage drop across the coil  
 $V_R(t)$  denote the voltage drop across the resistor  
 $V_C(t)$  denote the voltage drop across the capacitor  
 $V(t)$  denote the voltage *increase* across the power source

“Kirchoff’s Voltage Law” then states that

$$(1) \quad V = V_L + V_R + V_C$$

The circuit components are characterized by the relationship between the current flowing through them and the voltage drop across them:

$$(2) \quad \begin{array}{ll} \text{Coil :} & V_L = L\dot{I} \\ \text{Resistor :} & V_R = RI \\ \text{Capacitor :} & \dot{V}_C = (1/C)I \end{array}$$

The constants here are the “inductance”  $L$  of the coil, the “resistance”  $R$  of the resistor, and the *inverse* of the “capacitance”  $C$  of the capacitor. A very large capacitor, with  $C$  large, is almost like no capacitor at all; electrons build up on one plate, and push out electrons on the other, to form an uninterrupted circuit. We’ll say a word about the actual units below.

To get the expressions (2) into comparable form, differentiate the first two. Differentiating (1) gives  $\dot{V}_L + \dot{V}_R + \dot{V}_C = \dot{V}$ , and substituting the values for  $\dot{V}_L$ ,  $\dot{V}_R$ , and  $\dot{V}_C$  gives us

$$(3) \quad \boxed{L\ddot{I} + R\dot{I} + (1/C)I = \dot{V}}$$

This equation describes how  $I$  is determined from the impressed voltage  $V$ . It is a second order linear time invariant ODE. Comparing it with the familiar equation

$$(4) \quad \boxed{m\ddot{x} + b\dot{x} + kx = F}$$

governing the displacement in a spring-mass-dashpot system reveals an analogy between the two types of system:

<b>Mechanical</b>	<b>Electrical</b>
Mass	Coil
Damper	Resistor
Spring	Capacitor
Driving force	Time derivative of impressed voltage
Displacement	Current

8.2. **A word about units.** There is a standard system of units called the International System of Units, SI, formerly known as the mks (meter-kilogram-second) system. In terms of those units, (3) is correct when:

inductance  $L$  is measured in henries, H  
 resistance  $R$  is measured in ohms,  $\Omega$   
 capacitance  $C$  is measured in farads, F  
 voltage  $V$  is measured in volts, also denoted V  
 current  $I$  is measured in amperes, A

Balancing units in the equation shows that

$$\frac{\text{henry} \cdot \text{ampere}}{\text{sec}^2} = \frac{\text{ohm} \cdot \text{ampere}}{\text{sec}} = \frac{\text{ampere}}{\text{farad}} = \frac{\text{volt}}{\text{sec}}$$

Thus one henry is the same as one volt-second per ampere.

The analogue for mechanical units is this:

mass  $m$  is measured in kilograms, kg  
 damping constant  $b$  is measured in kg/sec  
 spring constant  $k$  is measured in kg/sec<sup>2</sup>  
 applied force  $F$  is measured in newtons, N  
 displacement  $x$  is measured in meters, m

Here

$$\text{newton} = \frac{\text{kg} \cdot \text{m}}{\text{sec}^2}$$

so another way to describe the units in which the spring constant is measured in is as newtons per meter—the amount of force it produces when stretched by one meter.